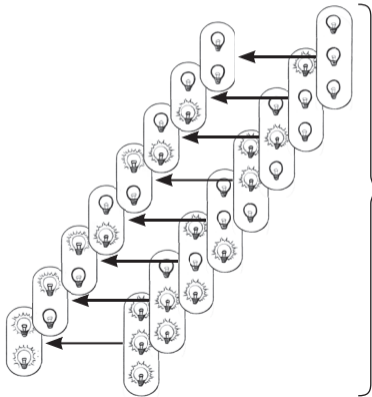


# Musterzuordnung



# Wahrheitstabelle

erster Summand	zweiter Summand	rechter Übertrag	linker Übertrag	Ergebnis
E1	E2	E3	A1	A2
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1